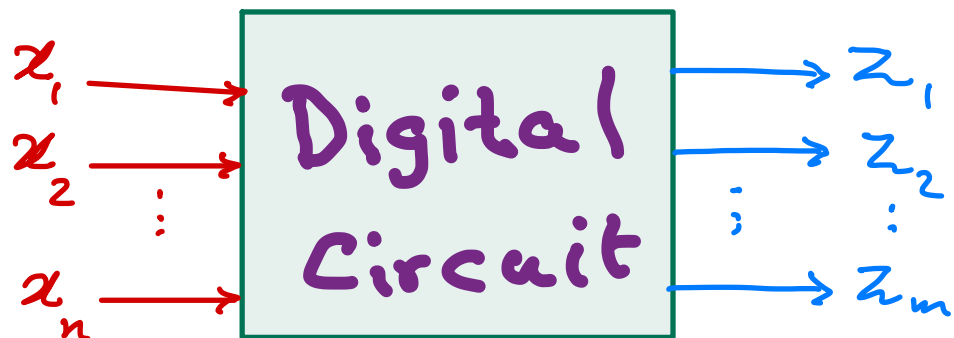


# Boolean Algebra

- \* Objective  $\rightarrow$  Study design of digital circuits
- \* Digital circuits use binary system
- \* Signals can be either Logic '0' or '1'  
Corresponding to High or Low voltages, resp.
- \* Physical value  $\rightarrow$  High/Low voltage
- \* Logic value  $\rightarrow$  1 / 0
- \* Digital circuits takes binary signals  
and produce binary signals:



\*  $x_i$  is input  $i$  to the circuit,  $z_i$  output  $i$

\* Generally,  $z_i = F(x_1, x_2, \dots, x_n) \rightarrow$  binary fun.  
 $\rightarrow$  Boolean fun.

Requires binary logic algebra

\* Binary logic algebra is commonly referred to as Boolean algebra, after G. Boole

\* Boolean functions take Boolean variables and produce Boolean output

\* To design digital circuits, we must know how to derive Boolean functions

\* Digital circuits implementing Boolean function is commonly referred to as logic circuit

\* Plan for the rest of the lesson:

- Def of Boolean Algebra
- Logic gates and operations
- Basic identities and duality principle
- Algebraic manipulations

# Definition of Boolean Algebra

- Algebraic structure with  $B = \{0, 1\}$ , two binary operators  $(\cdot, +)$ , and one unary operator  $(- \text{ or } ')$ , satisfying:

- \*  $\exists x, y \in B \text{ s.t. } x \neq y$

- \*  $\forall x \in B, \bar{x} \in B$

- \* closure under  $\cdot$  and  $+$

- \*  $0$  is identity for  $+$ ,  
 $1$  is identity for  $\cdot$ .

- \* Commutative under  $+$  and  $\cdot$ .

- \*  $\cdot$  is distributive over  $+$

- \*  $+$  is distributive over  $\cdot$ .

Usually  $+$  operator is OR

and  $\cdot$  operator is AND

the  $-$  unary operator is NOT

Ex 1

$$F = A \cdot B + 1$$

Diagram illustrating the components of the expression  $F = A \cdot B + 1$ :

- $A$  and  $B$  are labeled as **Variables** with arrows pointing to them.
- $\cdot$  and  $+$  are labeled as **operators** with arrows pointing to them.
- $1$  is labeled as **Constant** with an arrow pointing to it.

Operator precedence:


1. Parenthesis (if any) { Highest priority }
2. Not operator
3. AND operator
4. OR operator { Lowest priority }

# Logic Gates & Operations

\* In addition to representing logic circuits using Boolean algebra, we can represent them graphically

□ AND gate
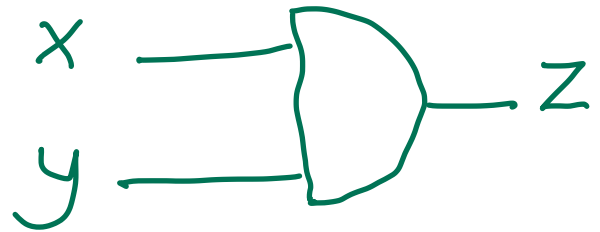
$$\begin{aligned} Z &= x \cdot y \\ &= xy \end{aligned}$$



Definition of AND using truth table


x	y	xy
0	0	0
0	1	0
1	0	0
1	1	1

Mathematically

$$xy = \begin{cases} 1 & \text{iff } x=1 \text{ and } y=1 \\ 0 & \text{otherwise} \end{cases}$$

## [2] OR gate

$$Z = x + y$$

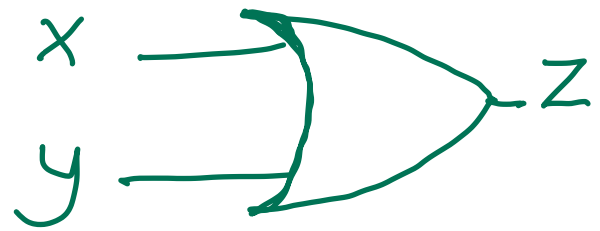

Definition of OR using truth table

x	y	x+y
0	0	0
0	1	1
1	0	1
1	1	1

Mathematically

$$x+y = \begin{cases} 1 & \text{iff } x=1 \text{ or } y=1 \\ 0 & \text{otherwise} \end{cases}$$

## [3] NOT gate

$$Z = \bar{x}$$



Definition of NOT gate using truth table

x	$\bar{x}$
0	1
1	0

Mathematically,

$$\bar{x} = \begin{cases} 0 & \text{iff } x=1 \\ 1 & \text{otherwise} \end{cases}$$


# Side Note

In addition to AND, OR, and NOT gates, there are other composite gates

## 1 NAND gate

AND followed by NOT

x	y	xy	(xy)'
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

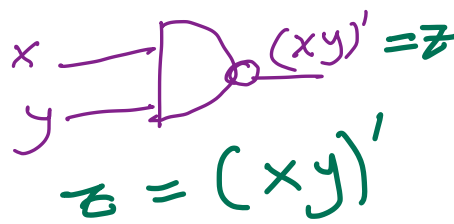


details later

## 2 NOR gate

OR followed by NOT

x	y	x+y	(x+y)'
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

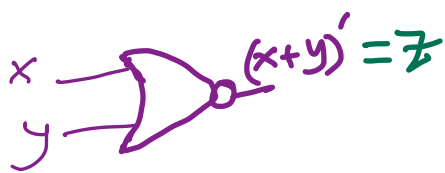

$$z = (x+y)'$$

## 3 XOR gate


$$z = x \oplus y = \begin{cases} 1 & \text{iff } x \neq y \\ 0 & \text{otherwise} \end{cases}$$

## 4 XNOR gate

$$(x \oplus y)' = \begin{cases} 1 & \text{iff } x = y \\ 0 & \text{otherwise} \end{cases}$$

Ex2  $F = a\bar{b} + b$

(a) Sketch the logic circuit of  $F$ .

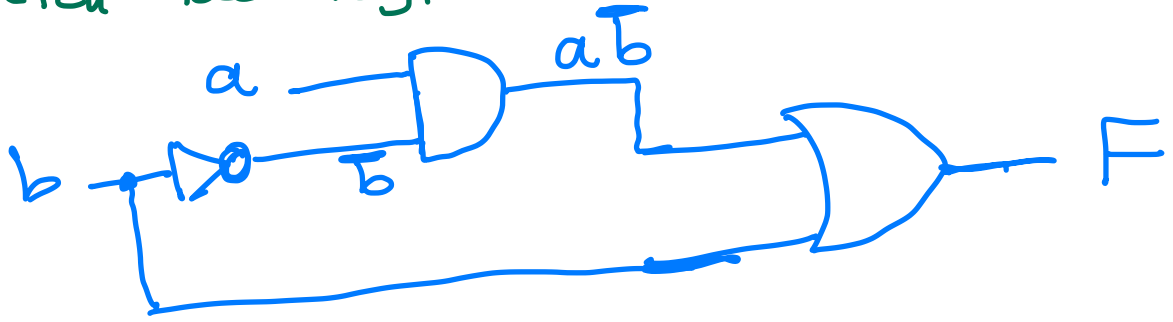

(b) Derive the truth table of  $F$


a	b	$\bar{b}$	$a\bar{b}$	F	$a+b$
0	0	1	0	0	0
0	1	0	0	1	1
1	0	1	1	1	1
1	1	0	0	1	1

(c) What can you say about  $F$ ?

$$F = a\bar{b} + b = a + b$$



### Ex3

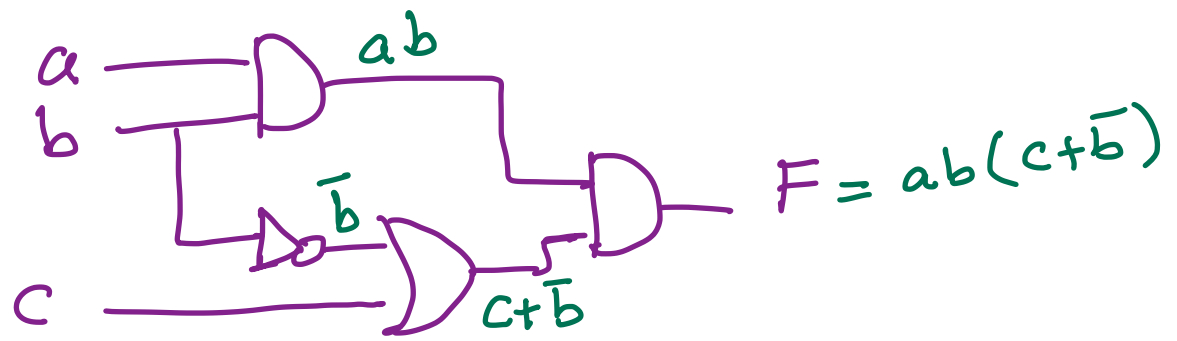

(a) Derive the Boolean expression of F.

(b) Derive the truth table of  $F = \underline{ab}(\underline{c + \bar{b}})$

a	b	c	$\bar{b}$	ab	$c + \bar{b}$	F	abc
0	0	0	1	0	1	0	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	0	0
0	1	1	0	0	1	0	0
1	0	0	1	0	1	0	0
1	0	1	1	0	1	0	0
1	1	0	0	1	0	0	0
1	1	1	0	1	1	1	1

$$\Rightarrow F = \underline{ab(c + \bar{b})} = \underline{abc}$$

# Basic Identities and Duality Principle

\* To obtain the dual expression of a given

expression  $\rightarrow$  change  $\cdot$  to  $+$   
 change  $+$  to  $\cdot$   
 change 1 to 0  
 change 0 to 1

<u>Prop. Name</u>	<u>Expression</u>	<u>Dual</u>
Identity	$x + 0 = x$	$x \cdot 1 = x$
Null	$x + 1 = 1$	$x \cdot 0 = 0$
Idempotence	$x + x = x$	$x \cdot x = x$
Complement	$x + \bar{x} = 1$	$x \cdot \bar{x} = 0$
Commutative	$x + y = y + x$	$xy = yx$
Associative	$(x + y) + z = x + (y + z)$	$(xy)z = x(yz)$
Distributive	$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$
Absorption	$x + xy = x$	$x \cdot (x + y) = x$
Minimization	$xy + \bar{x}y = y$	$(x + y)(\bar{x} + y) = y$
Simplification	$x + \bar{x}y = x + y$	$x \cdot (\bar{x} + y) = xy$
Consensus	$xy + \bar{x}z + yz = xy + \bar{x}z$	$(x + y)(\bar{x} + z)(y + z) = (x + y)(\bar{x} + z)$
DeMorgan's	$(x + y)' = \bar{x} \cdot \bar{y}$	$(xy)' = \bar{x} + \bar{y}$

# Algebraic Manipulations

- \* Use properties of Boolean algebra to minimize Boolean functions
- \* Minimization implies less hardware and less power consumption

Ex 4

Prove the Simplification Rule.

$$x + \bar{x}y = x + y$$

solution

$$\text{LHS} = x + \bar{x}y$$

$$= x \cdot 1 + \bar{x}y$$

$$= x(y + 1) + \bar{x}y$$

$$= xy + x \cdot 1 + \bar{x}y$$

$$= y(x + \bar{x}) + x$$

$$= y \cdot 1 + x$$

$$= x + y$$

$$= \text{RHS}$$

{identity}

{Null}

{dist.}

{dist. + ident}

{Null}

{comm.}

Ex 5

Prove consensus theorem

$$xy + \bar{x}z + yz = xy + \bar{x}z$$

$$\text{LHS} = xy + \bar{x}z + yz$$

$$= xy + \bar{x}z + (x + \bar{x})yz$$

{ ident. + complement }

$$= \underline{xy} + \underline{\bar{x}z} + \underline{xyz} + \underline{\bar{x}yz}$$

{ dist. law }

$$= xy(1+z) + \bar{x}z(1+y)$$

{ dist. law }

$$= xy + \bar{x}z$$

{ Null, ident. }

$$= \text{RHS}$$

---

Ex 6  $F = a'b(c' + d'c) + b(a + a'dc)$

Simplify  $F$  to a min. number of

literals. Justify every step.

$$F = a'b(c' + d'c) + b(a + a'dc)$$

$$= a'b(c' + d') + b(a + dc)$$

{ simplif. }

$$= b(a'(cd') + a + cd)$$

{ comm. + dist. + deMorg. }

$$= b((cd') + a + cd)$$

{ simplification }

$$= b$$

{ comp. + Null }

1 literal

Ex 7  $G = A\bar{B} + \bar{B}C + AB\bar{C} + AB$

Simplify to minimum number of literals.

$$G = A\bar{B} + \bar{B}C + AB\bar{C} + AB$$

$$= A(\bar{B} + B) + \bar{B}C + AB\bar{C}$$

{ dist. law }

$$= A + \bar{B}C + AB\bar{C}$$

{ comp. + AND identity }

$$= A(1 + B\bar{C}) + \bar{B}C$$

{ dist. law }

$$= A + \bar{B}C$$

{ AND/OR identities }

3 literals

Ex 8

Find and simplify the complement of

$$F = [(A\bar{B})' + C]\bar{D} + A\bar{C}$$

to minimum number of literals.

$$\overline{F} = \{ [(A\bar{B})' + C]\bar{D} + A\bar{C} \}'$$

$$= \{ [(A\bar{B})' + C]\bar{D} \}' \cdot \{ A\bar{C} \}' \quad \{ \text{DeMorgan's} \}$$

$$= ([ (A\bar{B})' + C ]' + D) \cdot (\bar{A} + C) \quad //$$

$$= (\bar{A}\bar{B}\bar{C} + D)(\bar{A} + C) \quad //$$

$$= \bar{A}(\bar{A}\bar{B}\bar{C} + D) + C(\bar{A}\bar{B}\bar{C} + D) \quad \{ \text{dist. law} \}$$

$$= \bar{A}D + CD$$

{ dist law + AND/OR id }

$$= (\bar{A} + C)D$$

{ dist. law }

3 literals

Ex 9 Given  $F = (A\bar{B} + C)\bar{D} + E$

without simplification, find

(a)  $\bar{F}$

$$\bar{F} = [(A\bar{B} + C)\bar{D} + E]'$$

$$= [(A\bar{B} + C)\bar{D}]' \bar{E}$$

{DeMorgan's}

$$= [(A\bar{B} + C)' + D] \bar{E}$$

$$= ((\bar{A} + B)\bar{C} + D) \bar{E}$$

(b) the dual of  $F$

$$F_{\text{dual}} = ((A + \bar{B})C + \bar{D})E$$

Note that the dual is similar to  $\bar{F}$  except for the complements.

### Ex 10

Simplify to min. literals

$$F = (A+B)(A+C)(\bar{A}+\bar{B})(A+\bar{C})$$

$$\begin{aligned} F &= (A+B)(A+C)(\bar{A}+\bar{B})(A+\bar{C}) \\ &= (A+BC\bar{C})(\bar{A}+\bar{B}) && \{\text{dist. law}\} \\ &= A(\bar{A}+\bar{B}) && \{\text{AND/OR identities}\} \\ &= A\bar{B} && \{\text{AND/OR id. + dist. law}\} \end{aligned}$$

2 literals

### Ex 11

Min. literals of  $F = A + \bar{A}C + (A+C)(\bar{A}+\bar{C})$

$$\begin{aligned} F &= A + \bar{A}C + (A+C)(\bar{A}+\bar{C}) \\ &= A + C + (A+C)(\bar{A}+\bar{C}) && \{\text{Simp.}\} \\ &= A + C && \{\text{Absorption}\} \end{aligned}$$

2 literals

Ex 12

simplify

$$F = AB + \bar{A}C + \bar{B}C + A\bar{C}$$

$$F = \underline{AB} + \underline{\bar{A}C} + \underline{\bar{B}C} + \underline{A\bar{C}}$$

$$= \underline{AB} + \underline{\bar{A}C} + \underline{BC} + \underline{\bar{B}C} + A\bar{C} + \underline{A\bar{B}} \quad \{\text{cons.}\}$$

$$= C(B + \bar{B}) + A(B + \bar{B}) + \bar{A}C + A\bar{C} \quad \{\text{dist.}\}$$

$$= C + A + \bar{A}C + A\bar{C}$$

$$= A + C + C + A$$

$$= A + C$$

{AND/OR id}

{comm., simp.}

{Idemp.}